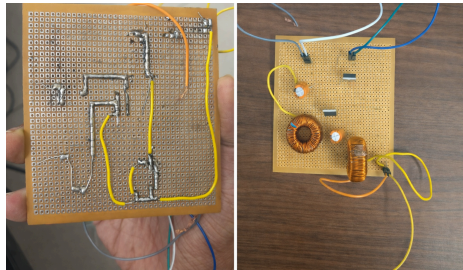


EE 252 LAB DC DC CONVERTER PROJECT REPORT


B1-G10 - ĆUK CONVERTER

DEVANSH CHAUDHARY	240002023
MAYUR SONI	240002037
ANKIT VERMA	240002008
BANDARU SHIVA	240002016

CIRCUITS



SOLDERED ĆUK CONVERTER ON
PERFBOARD

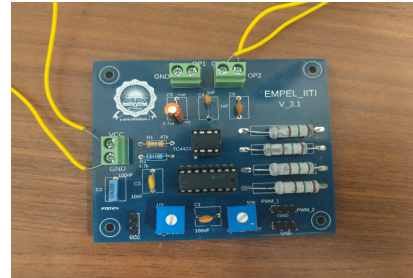

GATE DRIVER PCB


WAVEFORMS (Asked for in the Problem Statement)



INDUCTOR CURRENT (CCM)



INDUCTOR CURRENT (DCM)

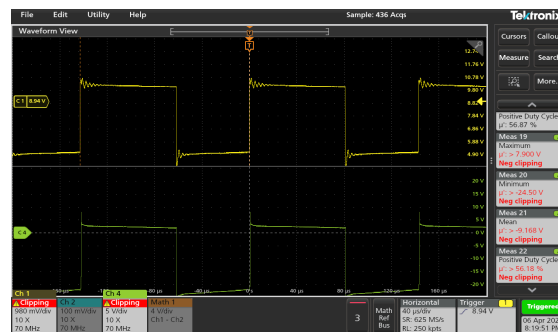

DIODE VOLTAGE (CCM)

VIDEO - [INCREASING LOAD RESISTANCE TO DEMONSTRATE DCM](#)