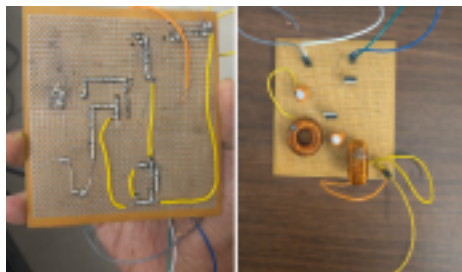


EE 252 LAB DC DC CONVERTER PROJECT REPORT

B1-G10 - ĆUK CONVERTER

DEVANSH CHAUDHARY	240002023
MAYUR SONI	240002037
ANKIT VERMA	240002008
BANDARU SHIVA	240002016

CIRCUITS




SOLDERED ĆUK CONVERTER ON GATE DRIVER PCB PERFBOARD

WAVEFORMS (Asked for in the Problem Statement)



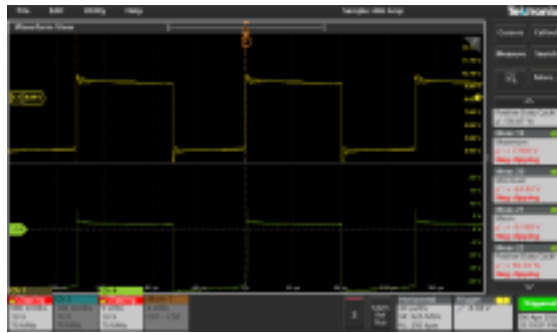INDUCTOR CURRENT (CCM) INDUCTOR
CURRENT (DCM)



DIODE VOLTAGE (CCM)

VIDEO - [INCREASING LOAD RESISTANCE TO DEMONSTRATE DCM](#)